

ASSIGNMENT-4(ALL PLOTS)

NAME: PRAFFUL CHOUDHARY

ROLL NUMBER: MT2021523

QUESTION 1 SOLUTION

SOLUTION IS OBTAINED BY USING ONLY 28 TRANSISTORS IN FULL ADDER .

